

Figure 1: Bootstrap Circuit

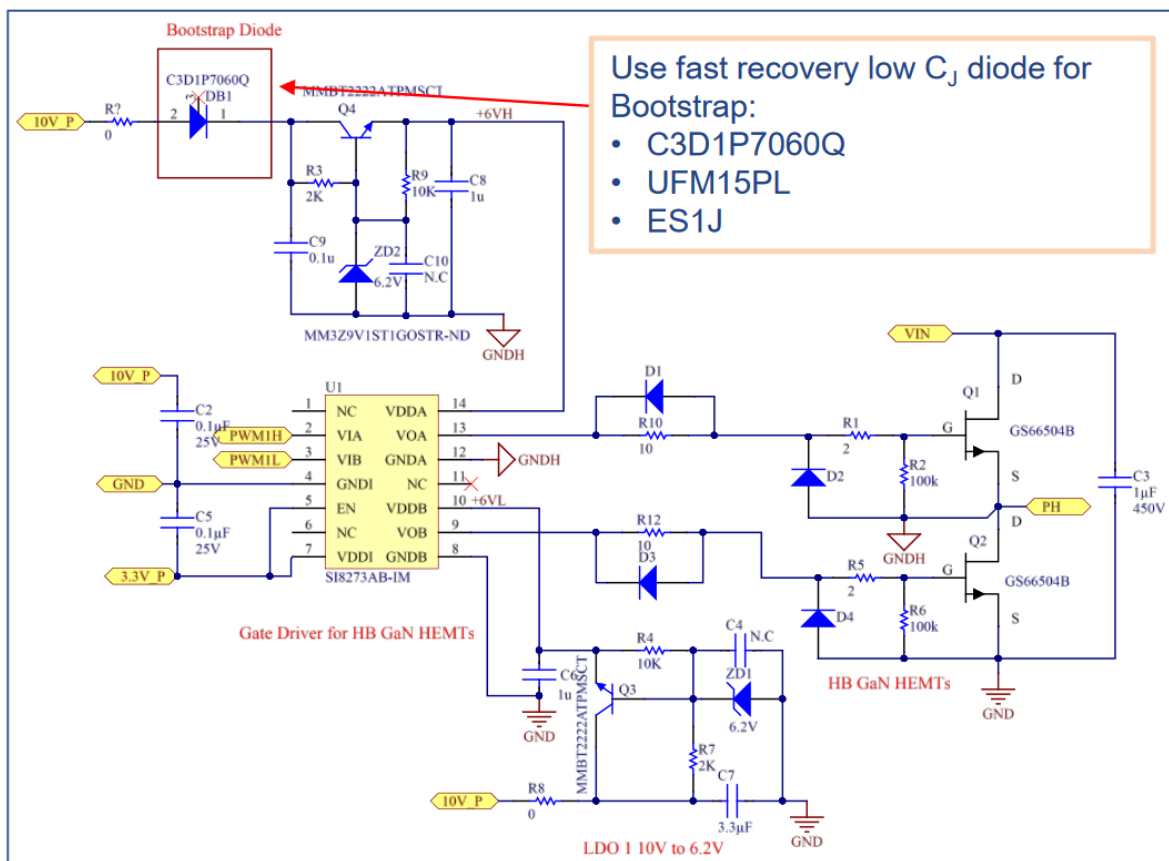


Figure 2: Recommended Bootstrap Driver

+ Simple Circuit just a capacitor-diode

+ PCB area

- 

Figure 3: Single Isolated Gate Driver